

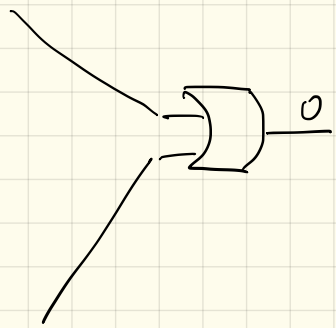


0

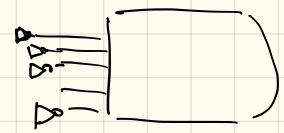

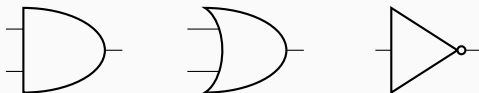- A function $F : \{0, 1\}^k \rightarrow \{0, 1\}$, where $k \in \mathbb{Z}^+$ is **arity** of F , is called a **Boolean function**
- Any Boolean function can be expressed as a combination of \wedge , \vee , \neg



- Do we need all three types of gates?


Boolean functions of arity 2

P	Q	\perp	\wedge	$\neg(p \Rightarrow q)$	p	$\neg q$	q	XOR \oplus	\vee
1	1	0	1	0	1	0	1	0	1
1	0	0	0	1	1	0	0	1	1
0	1	0	0	0	0	1	1	1	1
0	0	0	0	0	0	0	0	0	0


P	Q	$\neg \vee$	\Leftrightarrow	$\neg q$	\Leftarrow	$\neg p$	\Rightarrow	$\neg \wedge$	\top
1	1	0	1	0	1	0	1	0	1
1	0	0	0	1	1	0	0	1	1
0	1	0	0	0	0	1	1	1	1
0	0	1	1	1	1	1	1	1	1

Logic gates


■ AND, OR, NOT

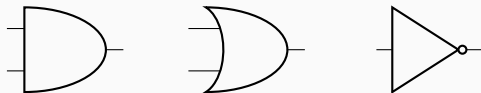

■ XOR

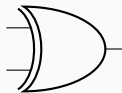

■ NAND, NOR, XNOR

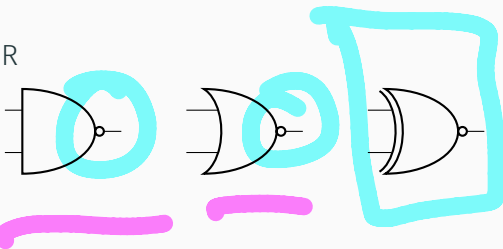

Universality of NAND and NOR

- NAND (AKA Sheffer stroke)
- and NOR (AKA Pierce arrow)

$$P \mid Q = \neg(P \wedge Q)$$


$$P \downarrow Q = \neg(P \vee Q)$$

are universal:


$$\neg P \equiv P \mid P$$



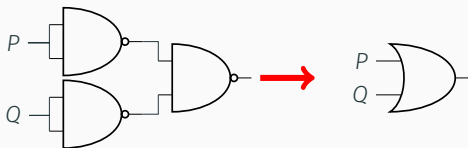
$$P \vee Q \equiv (P \mid P) \mid (Q \mid Q)$$


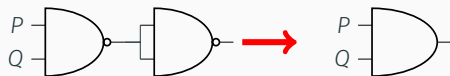
$$P \wedge Q \equiv (P \mid Q) \mid (P \mid Q)$$



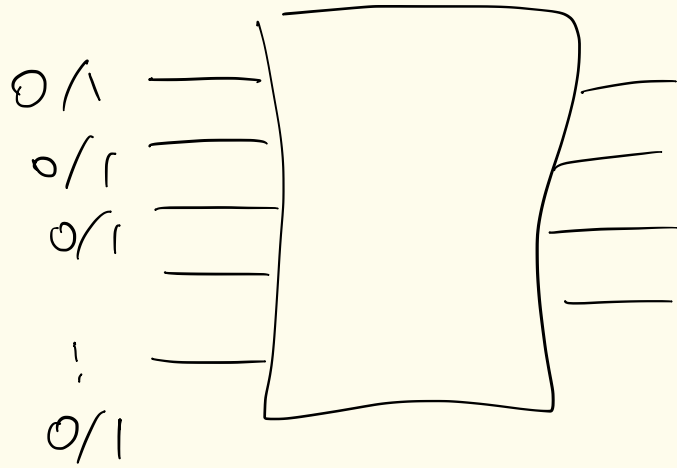Application: Number systems and circuits for addition



Positional system: multiply each digit by its place value

- Decimal notation:

$$4268_{10} = 4 \cdot 10^3 + 2 \cdot 10^2 + 6 \cdot 10^1 + 8 \cdot 10^0$$

- Binary notation

$$\begin{aligned} 1100\ 0111_2 &= 1 \cdot 2^7 + 1 \cdot 2^6 + 0 \cdot 2^5 + 0 \cdot 2^4 + 0 \cdot 2^3 + 1 \cdot 2^2 + 1 \cdot 2^1 + 1 \cdot 2^0 \\ &= 128 + 64 + 0 + 0 + 0 + 4 + 2 + 1 = 199_{10} \end{aligned}$$

*Here indices 10 and 2 are used to highlight the **base** of the number system*

$$0111_2 = 0 \cdot 2^4 + \underbrace{1 \cdot 2^3}_8 + \underbrace{1 \cdot 2^2}_4 + \underbrace{1 \cdot 2^1}_2 + \underbrace{0 \cdot 2^0}_0 = 8 + 4 + 2 = 14_{10}$$

Convert decimal numbers to binaries: divide by 2

Rule: divide repeatedly by 2, writing down the remainder from each stage from **right to left**.

Example:	$533/2 = 266$	remainder = 1
	$266/2 = 133$	remainder = 0
	$133/2 = 66$	remainder = 1
	$66/2 = 33$	remainder = 0
	$33/2 = 16$	remainder = 1
	$16/2 = 8$	remainder = 0
	$8/2 = 4$	remainder = 0
	$4/2 = 2$	remainder = 0
	$2/2 = 1$	remainder = 0
	$1/2 = 0$	remainder = 1

$$533_{10} = 1000010101_2$$

- If you know powers of 2, continually subtract largest power value from the number

$$\begin{aligned}123_{10} &= 64 + (123 - 64) = 64 + 59 \\ &= 64 + 32 + (59 - 32) = 64 + 32 + 27 \\ &= 64 + 32 + 16 + (27 - 16) = 64 + 32 + 16 + 11 \\ &= 64 + 32 + 16 + 8 + (11 - 8) = 64 + 32 + 16 + 8 + 3 = \\ &= 64 + 32 + 16 + 8 + 2 + (3 - 2) \\ &= 64 + 32 + 16 + 8 + 2 + 1 = \\ &= 1 \cdot 2^6 + 1 \cdot 2^5 + 1 \cdot 2^4 + 1 \cdot 2^3 + 0 \cdot 2^2 + 1 \cdot 2^1 + 1 \cdot 2^0 = \\ &= 1111011_2\end{aligned}$$

Binary addition

$$0_2 + 0_2 = 0_2$$

$$0_2 + 1_2 = 1_2$$

$$1_2 + 0_2 = 1_2$$

$$1_2 + 1_2 = 10_2$$

$$\begin{array}{r} \\ \\ + \\ \hline 1 \end{array}$$

$$\begin{array}{r}
 \overset{1}{1} \overset{1}{1} \overset{0}{0} \overset{0}{0} \overset{1}{1} \\
 + \quad \overset{1}{1} \overset{0}{0} \overset{1}{1} \overset{0}{0} \overset{1}{1} \\
 \hline
 \overset{1}{1} \overset{0}{0} \overset{1}{1} \overset{1}{1} \overset{0}{0} \overset{2}{2}
 \end{array}$$

$$A - B = C$$

$$\begin{array}{r}
 \overset{1}{1} \overset{1}{1} \overset{0}{0} \overset{0}{0} \overset{1}{1} \quad A \\
 - \quad \overset{1}{1} \overset{0}{0} \overset{1}{1} \overset{1}{1} \quad B \\
 \hline
 \overset{0}{0} \overset{0}{0} \overset{0}{0} \overset{1}{1} \overset{0}{0} \quad C
 \end{array}$$

$$A = B + C$$

$$\begin{array}{r}
 \overset{1}{1} \overset{0}{0} \overset{1}{1} \overset{1}{1} \\
 + \quad \overset{0}{0} \overset{0}{0} \overset{0}{0} \overset{1}{1} \\
 \hline
 \overset{1}{1} \overset{1}{1} \overset{0}{0} \overset{1}{1}
 \end{array}$$

$a_7 a_6 a_5 a_4 a_3 a_2 a_1 a_0$

A

$b_7 b_6 b_5 b_4 b_3 b_2 b_1 b_0$

B


2^{16}


a_7	---	a_0	b_7	---	b_0	c_8	c_7	---	c_0
-		-	-		-	-	-		-
-		-	-		-	-	-		-
-		-	-		-	-	-		-
-		-	-		-	-	-		-

Half-adder

$$\begin{array}{r} \\ \\ + \\ \hline \\ 1 \end{array}$$

P	Q	Carry	Sum
1	1	1	0
1	0	0	1
0	1	0	1
0	0	0	0

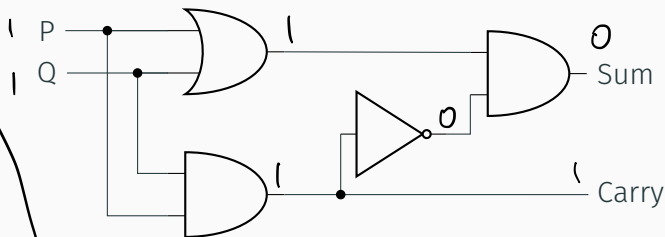

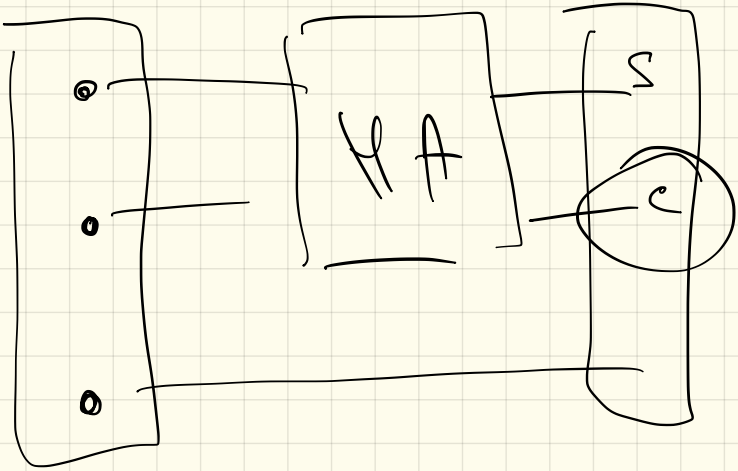


o

o



o

Full-adder

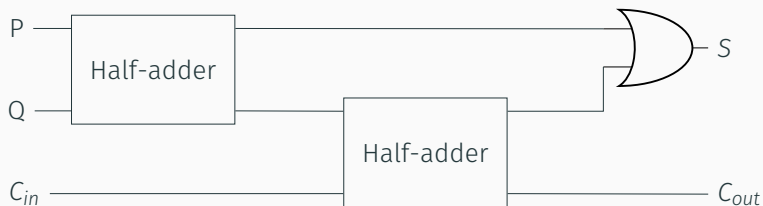

P	Q	C_{in}	C_{out}	S
1	1	1	1	1
1	1	0	1	0
1	0	1	1	0
1	0	0	0	1
0	1	1	1	0
0	1	0	0	1
0	0	1	0	1
0	0	0	0	0


'Black box' notation

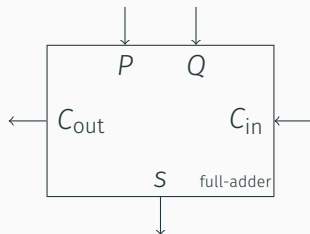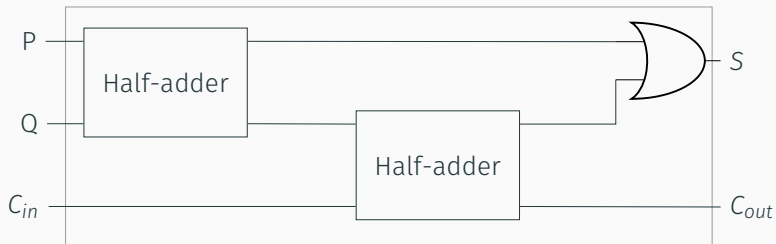


4-bit adder





$$\begin{array}{r}
 \\
 \\
 + \\
 \hline
 c
 \end{array}$$

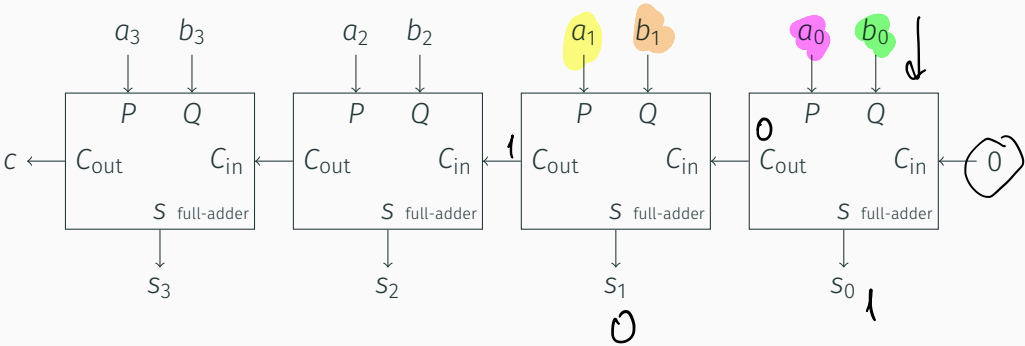
$$\begin{array}{r}
 \\
 \\
 + \\
 \hline
 1
 \end{array}$$



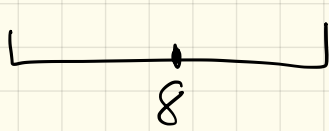


00000000
 0_{10}

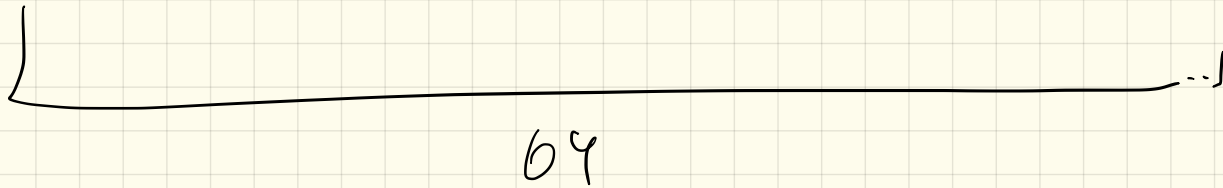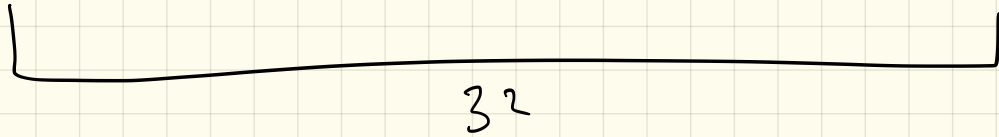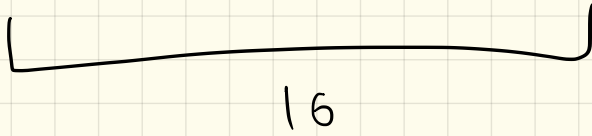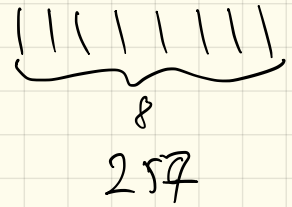

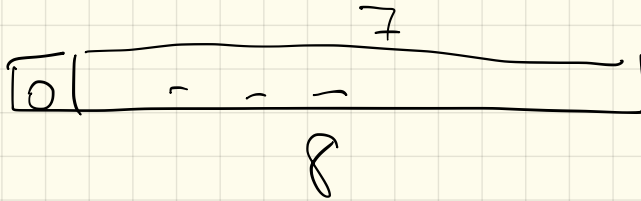

+ 127

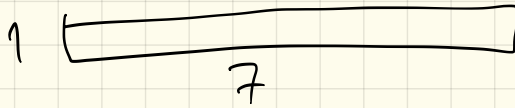

- 127

0 0000000 0 + 0

1 0000000 0 ~ 0

Computer representation of negative integers

- Typically a fixed number of bits is used to represent integers: 8, 16, 32 or 64 bits
 - **Unsigned** integer can take all space available
- Signed integers
 - **Leading sign**

$$0\ 000\ 0001_2 = 1_{10}$$

$$1\ 000\ 0001_2 = -1_{10}$$

but then

$$1\ 000\ 0000_2 = -0_{10} \text{ (?)}$$

- **Two's complement:**

given a positive integer a , the **two's complement** of a relative to a fixed **bit length** n is the binary representation of

$$2^n - a.$$